4/23/2014 EE225_Lab2

```
% Circuits III Lab 2
clear
format SHORT
syms t s
R1 = 4000;
R2 = 10000;
R3 = 5000;
C1 = 0.2*10^{-6};
C2 = 0.4*10^{-6};
Vc1 = 5;
Vc2 = 5;
vint = [20 + 5*cos(2*pi*200*t)]*heaviside(t);
Vins = laplace(vint,t,s);
pretty(Vins)
A = [(R1+1/(s*C2)+R3) - (1/(s*C2)+R3); - (1/(s*C2)+R3);
B = [Vins-(Vc2/s);0];
Soln = inv(A)*B;
simplifyFraction(Soln)
Vos = R2*Soln(2);
pretty(simplify(Vos))
vot = ilaplace(Vos,s,t)
```

4/23/2014 EE225_Lab2

vot =

 $\begin{array}{l} (\exp{(-(295147905179352825856*t)/1298650782789152375)} * (9333096161056214253327044437219178493322406137298583984375*pi^2 + 4017345110647475507062453527010741785632257210109132800000)) / (1298650782789152375*(1054058659774298889027859981855087890625*pi^2 + 340282366920938463463374607431768211456)) - (1361129467683753792259819967610880000000*pi*sin(400*pi*t) - 2395587863123406565972409049670654296875*pi^2*cos(400*pi*t)) / (1054058659774298889027859981855087890625*pi^2 + 340282366920938463463374607431768211456)) \end{array}$

Published with MATLAB® R2013b